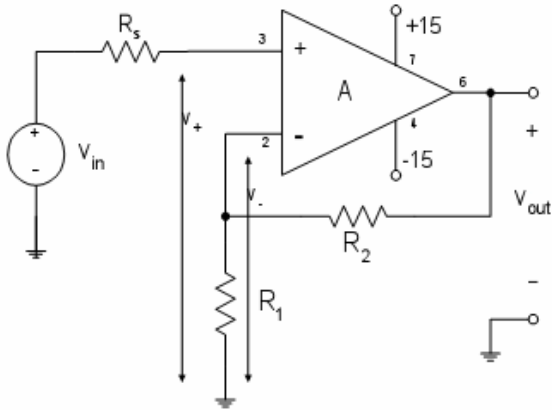


同相放大器增益分析

使用有限开环增益例子

参考图 7 的 Motorola MC 1741C 特性：开环频率响应



$$\begin{aligned} \text{令 } R_s = 0; \text{ 因此 } v_+ &= v_{in} \\ v_- &= \frac{R_1}{R_1 + R_2} \times v_{out}; \text{ 但 } v_+ = v_- \\ \text{所以 } v_{in} &= \frac{R_1}{R_1 + R_2} \times v_{out}; \\ \frac{v_{out}}{v_{in}} &= \frac{R_1 + R_2}{R_1} \\ \text{或 } A_v &= 1 + \frac{R_2}{R_1} \end{aligned}$$

无限大开环增益分析

1 Hz, 1000 Hz, 和 10kHz 处的例子

电压增益 $A_v = 40\text{dB} = 100$; $R_2 = 100\text{k}\Omega$, $R_1 = 1\text{k}\Omega$; [OK $101 = 40.1\text{dB}$!]

1. 在 1 Hz 处, $A_{vol} = 100\text{ dB} = 1 \times 10^5 = 100,000$.

$$A_v = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 10^5 \times 0.01} = \frac{10^5}{10^3} = 100 = 40\text{dB}$$

注意: $A_\beta = 10^3 = 60\text{ dB}$; 60 dB 开环增益 + 40 dB 闭环增益 = 100 dB 总增益

2. 在 1000 Hz 处, $A_{vol} = 60\text{ dB} = 10^3 = 1000$.

$$A_v = \frac{A}{1 + A\beta} = \frac{10^3}{1 + 10^3 \times 0.01} = \frac{10^3}{10 + 1} = \frac{1000}{11} = 90.9 = 39.2\text{dB}$$

注意: $A_\beta = 10^1 = 20\text{ dB}$; 20 dB 开环增益 + 40 dB 闭环增益 = 60 dB 总增益

3. 在 10 kHz 处, $A_{vol} = 42\text{ dB} = 1.26 \times 10^2 = 126$.

$$A_v = \frac{A}{1 + A\beta} = \frac{126}{1 + 126 \times 0.01} = \frac{126}{1 + 1.26} = \frac{126}{2.26} = 55.8 = 34.9\text{dB}$$

注意: $A_\beta = 1.26 = 2.0\text{ dB}$; 2 dB 开环增益 + 40 dB 闭环增益 = 42 dB 总增益